

ECE533 – Closed-Loop Digital SMPS

Design Project

Student #1: Mubarek Abdela (1001027738)

Student #2: Alok Deshpande (999859309)

Date: 20/4/2018

Introduction

This report details the development of a synchronous boost converter with a digital controller implemented in an FPGA. Both the converter hardware and software components are designed and subsequently tested. The report has two sections. Part A details the open-loop design, simulation, and testing. Part B details the closed-loop control design and testing. The report concludes with a summary of the results showing that the controller meets specifications.

Part A

This part describes the open-loop design. After designing the hardware components, the design is simulated to determine the effect of load on duty cycle and efficiency, as well as to verify that it meets open-loop requirements. Finally, the experimental testing results are shown.

1) DC Analysis

Below, the DC analysis of the designed boost converter with inclusion of the non-idealities is presented. The ideal conversion ratio for a boost converter is:

$$M_{ideal}(D) = \frac{V_o}{V_g} = \frac{1}{D'}$$

However, considering the conduction losses, this ratio must be re-derived.

From IVSB on the inductor:

$$\langle v_L \rangle = D(V_g - I_L R_L - I_L R_{ON}) + D'(V_g - I_L R_L - I_L R_{ON} - V_o) = 0$$

Rearranging:

$$\frac{V_o}{V_g} = \frac{1}{D'} - \frac{I_L(R_L + R_{ON})}{D'V_g}$$

From CCB on the output capacitor:

$$\langle i_c \rangle = D \left(-\frac{V_o}{R} \right) + D' \left(I_L - \frac{V_o}{R} \right) = 0$$

This gives:

$$I_o = D' I_L$$

This gives the non-ideal conversion ratio to be:

$$M_{non-ideal}(D) = \frac{1}{D'} \left(\frac{1}{1 + \frac{R_L + R_{ON}}{R}} \right)$$

a. Range of Duty Cycle

By considering the output voltage to be at the nominal value of 32V, and heavy load operating current of 1 A and thus, 32Ω load resistance, the operating duty cycle range is obtained. The duty cycle should not be lower than:

$$\frac{(32V)}{(13V)} = \frac{1}{D'} \left(\frac{1}{1 + \frac{10.3m\Omega + 19m\Omega}{32}} \right)$$

$$D_{min} = 0.594$$

Similarly, the maximum duty-cycle would be: $D_{max} = 0.719$

Therefore, the range of allowable duty cycles is:

$$0.594 < D < 0.719$$

b. Range of Load Resistance

The load resistance is:

$$R = \frac{V_o}{I_o}$$

One can determine the maximum resistance by considering maximum output voltage for minimum output current:

$$R_{max} = \frac{(34.6V)}{(0.2A)} = 173\Omega$$

Likewise, the converse can be done to find the minimum resistance:

$$R_{max} = \frac{(29.5V)}{(1A)} = 29.5\Omega$$

Hence, the testing range of the load resistance is: $29.5\Omega < R < 173\Omega$

c. Efficiency due to conduction loss

From the above derivation of conversion ratios, the ideal and non-ideal conversion ratios were determined. Based on these, the efficiency is:

$$\begin{aligned}\eta &= \frac{M_{non-ideal}(D)}{M_{ideal}(D)} \\ &= \left[\frac{1}{D'} \left(\frac{1}{1 + \frac{R_L + R_{ON}}{R}} \right) \right] \div \left(\frac{1}{D'} \right) \\ &= \frac{1}{1 + \frac{R_L + R_{ON}}{R}}\end{aligned}$$

One may determine the lowest efficiency for the maximum output current, maximum input supply, and minimum duty cycle. Doing so gives a minimum efficiency of:

$$\begin{aligned}\eta &= 1 - \frac{(1A)(10.3m\Omega + 19m\Omega)}{(1 - 0.595)(13V)} \\ &\cong 0.967\end{aligned}$$

This meets the specification, and so the design is feasible.

2) **Component selection**

a. Output Capacitor

The main conduction losses is mainly affected by the equivalent series resistance (ESR) of the inductor resistance (R_L) and the transistor ON resistance (R_{ON}). For the selected components, these were determined to be $R_L = 10.3m\Omega$ and $R_{ON} = 19m\Omega$.

To determine the minimum value of C_{out} , one need just meet the output voltage ripple specification:

$$\begin{aligned}I_O &= C_{out} \frac{dV_o}{dt} \\ &= C_{out} \frac{2\Delta V_o}{DT_s}\end{aligned}$$

$$C_{out} = \frac{I_o}{\Delta V_o} \frac{D}{2f_s}$$

The switching frequency of 150k Hz was selected and the value of C_{out} was maximized to ensure successful operation under the worst condition as shown below:

$$\begin{aligned} C_{out_{min}} &= \frac{(1A)}{(350mV)} \frac{(0.7182)}{2(150kHz)} \\ &\cong 19.75\mu F \end{aligned}$$

Hence, this is the minimum capacitance required. Based on the calculation and component tolerance a $22\mu F$ capacitor was chosen.

b. Inductor

The inductor was selected to ensure operation in CCM under all conditions:

$$I_L = \Delta i_L$$

$$\frac{I_o}{D'} = \frac{V_g}{L} \frac{D}{2f_s} \Rightarrow L = \frac{V_g D' D}{I_o 2f_s}$$

$$\begin{aligned} L &= \frac{(13V)}{(0.2A)} \frac{(1 - 0.595)(0.595)}{2(150kHz)} \\ &\cong 56\mu H \end{aligned}$$

Based on the above calculation, and components available on Digi-Key, a $68\mu H$ inductance was chosen.

c. Transistor

The RMS current $i_{Q,RMS}$ is given by:

$$i_{Q,RMS} = I_L \sqrt{D \left(1 + \frac{1}{3} \left(\frac{\Delta i_L}{I_L} \right)^2 \right)}$$

The DC component is given by:

$$I_L = \frac{I_o}{D'}$$

This value is maximized at the maximum duty cycle and output current so:

$$I_{Lmax} = \frac{(1A)}{(1 - 0.718)} \cong 3.56A$$

For the selected inductance, the maximum ripple is:

$$\begin{aligned} \Delta i_L &= \frac{V_g}{L} \frac{D}{2f_s} \\ &= \frac{(13V)}{(68\mu H)} \frac{(0.718)}{2(150kHz)} \\ &\cong 0.490A \end{aligned}$$

Hence, the RMS transistor current is:

$$\begin{aligned} i_{Q,peak} &= I_L \sqrt{D \left(1 + \frac{1}{3} \left(\frac{\Delta i_L}{I_L} \right)^2 \right)} \\ &\cong 3.02A \end{aligned}$$

The peak voltage across the high-side transistor is V_{out} . Hence, the transistors should be rated above 34.6V. In addition, by considering the switching frequency, the gate driver current and Figure of Merit (FOM), two transistors with the same data sheet were selected (i.e. rated voltage of 60 V, rated current of 7A, R_{on} of 19m Ω and gate charge of 20nC).

d. Gate driver selection:

The gate driver must charge equal gate capacitances (having selected the same transistors), but the required charging time differs, based on the duty cycle.

For a switching frequency of $T_{sw} = \frac{1}{150kHz} = 6.67\mu s$, each transistor is ON for its duty cycle time.

For M0, this is at minimum:

$$D_{min} T_{sw} = (0.595)(7.14\mu s) \cong 4.25\mu s$$

Whereas for the transistor M1:

$$D'_{min} T_{sw} = (1 - 0.718)(7.14\mu s) \cong 2.01\mu s$$

Choose the transistors to turn within a very short period of this time (e.g. 50x faster switching). These periods are, respectively for M0 and M1:

$$t_0 \cong 85ns \text{ and } t_1 \cong 40ns$$

The gate capacitances must charge to $V_{gs,min}$, which is chosen more than the threshold voltage in order to turn on the transistors with low R_{ON} . Knowing the gate charge $Q_{gs,min}$ associated with $V_{gs,min} = 10V$ from the datasheet of the transistor, one can determine the required driver output current to charge the gate within a time Δt as:

$$I_{drive} = \frac{Q_{gs,min}}{\Delta t}$$

For $Q_{gs,min} = 20nC$, as indicated in the MOSFET datasheet, the required output currents for the low-side and high-side drivers are to charge within times $\Delta t = t_0 \cong 85ns$ and $\Delta t = t_1 \cong 40ns$, respectively. These calculations give the required output currents to be, respectively:

$$I_{drive,0} \cong 394mA \text{ and } I_{drive,1} \cong 832mA$$

Choosing the higher of these two values, this means that the gate driver must be able to provide at least this much output current.

e. Bootstrap circuit design

The bootstrap design was done based on the theory presented in one application note [1].

The minimum capacitance in the bootstrap circuit depends on the charge that it must store to supply the driver (Q_{cb}), and the voltage the high side driver must provide this charge at (ΔV_{boot}).

The charge Q_{cb} must be sufficient to charge the gate capacitance and then ensure the gate driver supplies its quiescent current (I_{supply}) to keep the driver voltage ON for a period of at most $D_{max}T_{sw}$. Hence, the charge is calculated to be:

$$\begin{aligned} Q_{cb} &= Q_{gs,min} + D_{max}T_{sw}I_{supply} \\ &= (20nC) + (0.718)(7.14\mu s)(2.6mA) \\ &\cong 33.3nC \end{aligned}$$

The voltage at which this must then be supplied is equal to the maximum allowable change in voltage across the capacitance during a switching cycle (i.e. maximum ripple), since:

$$\Delta Q = Q_{cb} = C_b \Delta V_{boot}$$

The maximum ripple is chosen to be an arbitrarily small value as is done in [1] (2% of the DC gate drive voltage), so it is:

$$\begin{aligned}\Delta V_{boot} &= 0.02V_{drive} \\ &= 0.02(10V) \\ &= 0.2V\end{aligned}$$

Note that here the DC drive voltage was taken to be 10V, since that is the value in the range of input voltages for which the low R_{ON} design has been developed, as previously mentioned.

Knowing Q_{cb} and ΔV_{boot} , the bootstrap capacitance is:

$$\begin{aligned}C_{b,min} &= \frac{Q_{cb}}{\Delta V_{boot}} \\ &= \frac{(33.3nC)}{(0.2V)} \\ &\cong 0.23\mu F\end{aligned}$$

The actual value used was 0.23uF.

Note that: the selected gate driver needs no additional bootstrap diode or resistor.

3) Summary

The following table summarizes the selected components:

<u>Table 1: Specifications of Selected Components</u>		
Parameter	Value	Unit
L	68	μH
R_l	10.3	$m\Omega$
$R_{on1} @ V_{in,min}$	19	$m\Omega$
$R_{on2} @ V_{in,min}$	19	$m\Omega$
$Q_{gt1} @ V_{in,min}$	20	nC
$Q_{gt2} @ V_{in,min}$	20	nC
C_{out}	22	μF
$Volume\ of\ L + C$	14350+399=14750	mm^3
$Cost\ of\ L+C$	9784.36	\$/ 1000 units

Table 2: Selected Components	
Component	Digikey/Newark Part #
Gate driver IC	296-46403-1-ND
L	732-11714-ND
M_1	785-1438-5-ND
M_2	785-1438-5-ND
C_{out}	493-9884-1-ND

4) Simulation of the Design

The following test setup was used to verify that the steady-state conditions met the specification, and to estimate the conduction loss in the setup. Note that the only the parasitic losses associated with the on resistance of the MOSFETs and the ESR of the output capacitor and inductor were modelled. The switching losses and losses due to the gate driver and sensors were not modeled.

a. Duty Cycle ($V_{in}=9V$ and $V_{in}=14V$)

Ideally, for load variations, there should be no need to change duty cycle to maintain constant output voltage (i.e. constant conversion ratio). However, when the converter is non-ideal, this is no longer the case.

Based on this setup, the variation in duty cycle with load current was first simulated to estimate the effect of some of the parasitic. Upon simulating, the following results were obtained:

 


Figure 1: Variation in duty cycle (simulation only)

This shows a higher duty cycle is required to maintain the same conversion ratio as conduction losses increase.

b. Output voltage ripple

The output voltage ripple was one steady-state requirement to meet. Upon testing it in simulation at all combinations of the extreme cases of load and duty cycle, the following results were obtained:

<u>Table 3: Measured output voltage ripple</u>			
		Output Voltage Ripple (V)	
		<u>Output Current: 0.1A</u>	<u>Output Current: 1A</u>
<u>Supply</u>	9	0.027V	0.26V
<u>Voltage (V)</u>	14	0.03V	0.2V

This shows the ripple requirement (ripple less than 0.35V) is theoretically met under all conditions.

c. Efficiency (Vin=9V and Vin=14V)

The other requirement tested was the efficiency, only accounting for conduction since other losses were not modelled. By simulating under different load conditions in the same was as done in experimental testing, the following result was obtained:

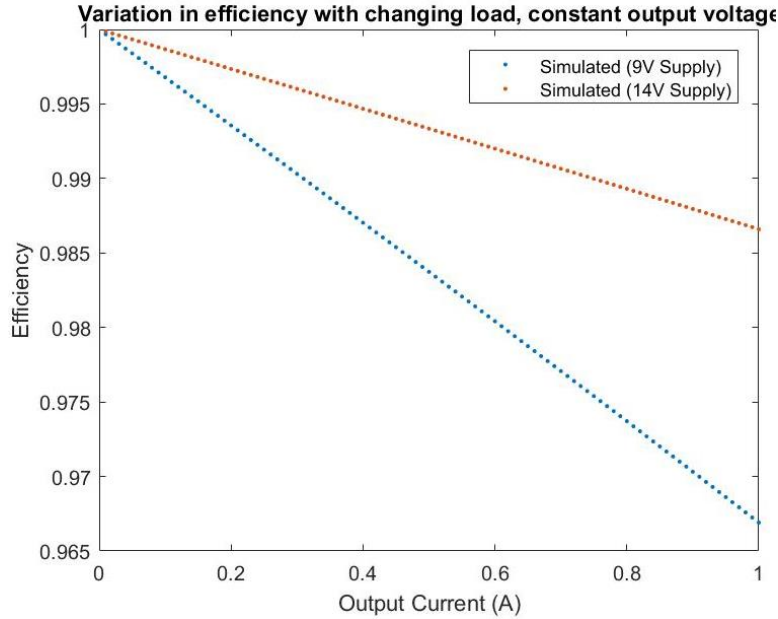


Figure 2: Variation in efficiency (simulation only)

This graph shows that the conduction loss is extremely minimal. It also shows that conduction loss increases with duty cycle and load, as expected. There is also higher efficiency at high supply voltage, which is reasonable because the current is reduced at higher input voltage for constant output voltage.

Note that the efficiency approaches 100% in the simulation for the case of no output current because the simulation only captures conduction losses. In actuality, the efficiency drops at light load due to the dominance of switching loss, as can be seen in the next section. Furthermore, the curve appears to be linear, but it would be non-linear if the switching losses were to be included

5) Experimental Testing

a. Duty Cycle ($V_{in}=9V$ and $V_{in}=14V$)

This test was done by varying the load resistance to achieve a particular output current, and varying D to achieve a fixed V_{out} of 32V. The duty cycle was adjusted by using the switches in FPGA. Figure 4 shows the experimental results, alongside the simulation results for comparison:

 


Figure 3: Variation in duty cycle (simulated and experimental)

These results show that the duty cycle varies very little with output current, just as in the simulated case. The experimental and simulation results deviate slightly, since switching and gate driver losses are not included. For the small variation that is present, this also shows that a higher duty cycle is required to produce the same amount of output current.

b. Efficiency ($V_{in}=9V$ and $V_{in}=14V$)

The efficiency of the converter was tested at different load at a fixed output voltage of 32V. Figure 4 shows the results:

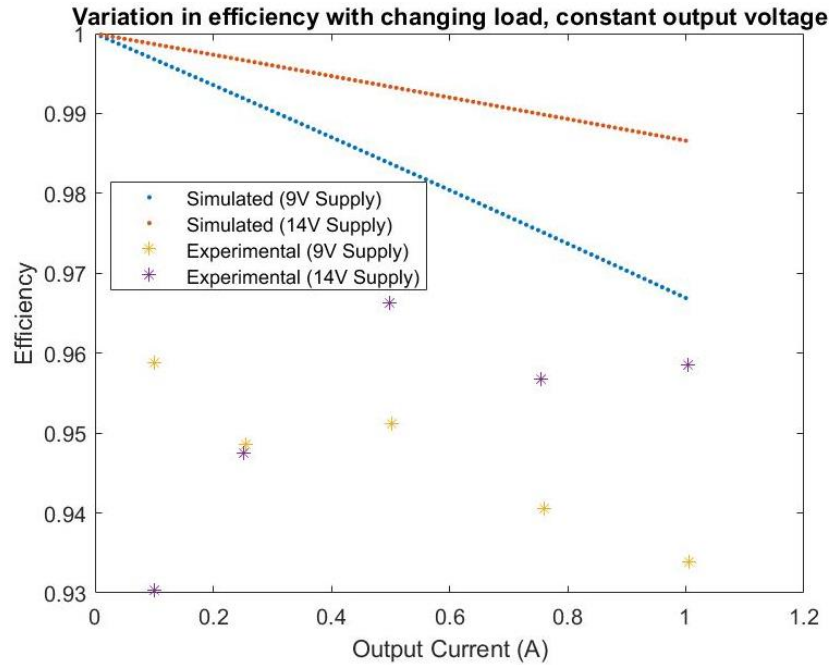


Figure 4: Variation in efficiency (simulated and experimental)

Firstly, this shows that under all load and supply conditions, the efficiency is great than 93% (thus, the specification is always met). It also shows that at low supply voltage, the conduction loss dominates, whereas at high supply voltage the conduction loss is reduced since the input current is lower.

c. Output voltage ripple (for $V_{in}=14V$ and $I_{out}=0.1A$)

The ripple was measured at one condition of load (0.1 A) and supply (14V). The following plot shows the peak-to-peak output voltage ripple (130mV) is less than the specification (350mV) even experimentally.

 


Figure 5: Output voltage ripple

The period of the ripple was also measured:

 


Figure 6: Output voltage ripple, showing switching period

The period is found to correspond to a frequency of $f = \frac{1}{6.7\mu s} = 150kHz$, which matches the switching frequency. This confirms that the viewed waveform is indeed the ripple, and not noise.

Note that in the above figures, the DC voltage has been filtered out, clearly show the ripple.

d. Soft start testing

Soft start was implemented for this converter by initially operating in open-loop mode until the output voltage reached the specified value. The duty cycle was ramped linearly to prevent overshoot in the output voltage. (This would otherwise occur during the transience of closed-loop startup.) The following figure shows the ramp in output voltage as the duty cycle increases over a period of 250ms.

 


Figure 7: Output voltage during soft start

Part B

1) Sensor Design

Output Voltage Sensing

As shown in Appendix A, the output voltage sensor is a resistive divider with a capacitor in parallel to reduce noise at high frequency. Hence, the DC gain is:

$$K_{sense} = \frac{R_7}{R_7 + R_8}$$

And the pole must be:

$$\omega_{sense} = \frac{1}{C(R_7 || R_8)}$$

This gives a transfer function of:

$$\begin{aligned} H_{sense}(s) &= \frac{K_{sense}}{1 + \frac{s}{\omega_{sense}}} \\ &= \frac{R_7}{R_7 + R_8} \cdot \frac{1}{1 + sc(R_7 || R_8)} \end{aligned}$$

The resistors were selected to step down the output voltage from its DC value (nominally 32V) to the reference value of the ADC (3.5V). To achieve this, resistor values of $R_7 = 80.6k\Omega$ and $R_8 = 10k\Omega$ were chosen.

$$K_{sense} = \frac{R_7}{R_7 + R_8} = \frac{3.5}{32}$$

It is also desired to reduce the power loss due to the sensor resistors, so the resistors should be chosen to be large.

The capacitance C_2 was chosen to be 1nF. This gives a pole of $\omega_{sense} = 112.41 \text{ k rad/s}$.

Based on these values, the sensor transfer function is:

$$H_{sense}(s) = \frac{0.1104}{8.896 \times 10^{-6}s + 1}$$

Sensor design for the input voltage is given in Appendix B.

2) Controller Design

In order to design a compensator, the small-signal model of the converter is derived as shown in Appendix B and based on the analysis, the following control to output transfer function was obtained.

$$G_{vd}(s) = \frac{\left(\frac{1}{sC} + R_c\right) \parallel R_{load} \left(\frac{V_o}{D'}\right)}{\left(\frac{1}{sC} + R_c\right) \parallel R_{load} + \frac{sL}{D'^2} + \frac{R_L + R_{on}}{D'^2}} - I_L \left(\frac{sL + R_L + R_{on}}{D'^2} \parallel \left(\frac{1}{sC} + R_c\right) \parallel R_{load} \right)$$

The plant transfer function $G_{vd}(s)$ of the converter is plotted using MATLAB as shown below.

 


Figure 8: control to output transfer function

The controller was designed for the worst case (9V input voltage and 1A output current) operating conditions. Given the above transfer function, the PWM gain and the output sensor transfer function, the uncompensated open-loop gain is:

$$T(s) = \frac{1}{V_m} G_{vd}(s) H_{sense}(s)$$

Bode plot of the uncompensated system is given in Figure 9 and the figure shows that the system is unstable.

 


Figure 9: Bode plot of the uncompensated open-loop transfer function

The controller was designed using SISOTOOL in MATLAB to achieve a phase margin above 45° and a crossover frequency below one-tenth of the switching frequency. Furthermore, the sampling frequency of the ADC was taken into consideration. A PID controller meeting the specifications was designed and the transfer function is given below:

$$G_c(s) = \frac{34.246(s^2 + 2976s + 2.318 \times 10^6)}{s(s + 5.34 \times 10^5)}$$

The plots obtained from SISOTOOL, which includes the compensated system in Figure 10.

 


Figure 10: The results from SISOTOOL.

The controller achieves a phase margin of 57.5° , infinite DC gain and a crossover frequency of $1.08 \times 10^4 \text{ rad/s}$, which is much less than the switching frequency of 150 kHz, but still it could provide a reasonably fast response.

Since we need a digital controller, a bilinear transformation of the compensator transfer function was obtained by using a sampling frequency of 250 kHz as shown below:

$$G_c = \frac{34.246(z^2 - 1.995z + 0.9951)}{(z - 1)(z - 0.1181)}$$

Upon taking the inverse transform, the resulting compensator in the time domain is:

$$d(t + 1) = 1.1181d(t) - 0.1181d(t - 1) + 34.246(e(t) - 1.995e(t - 1) + 0.9951e(t - 2))$$

3) Experimental and Simulation Test Results

The discrete controller was tested by using a code in MATLAB with PLECS block-set and Figure 11 given bellow shows the block diagram used for testing the controller.

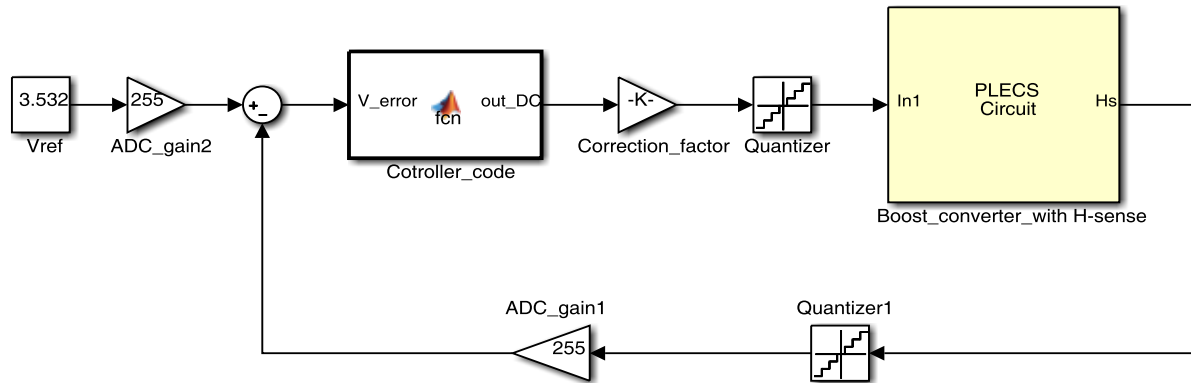


Figure 11: The block used for testing the discrete controller.

In addition, the variation of phase margin of the controller with the supply/input voltage and the output load is given in Figure 12. The figure shows that the controller meet the specification under all conditions.

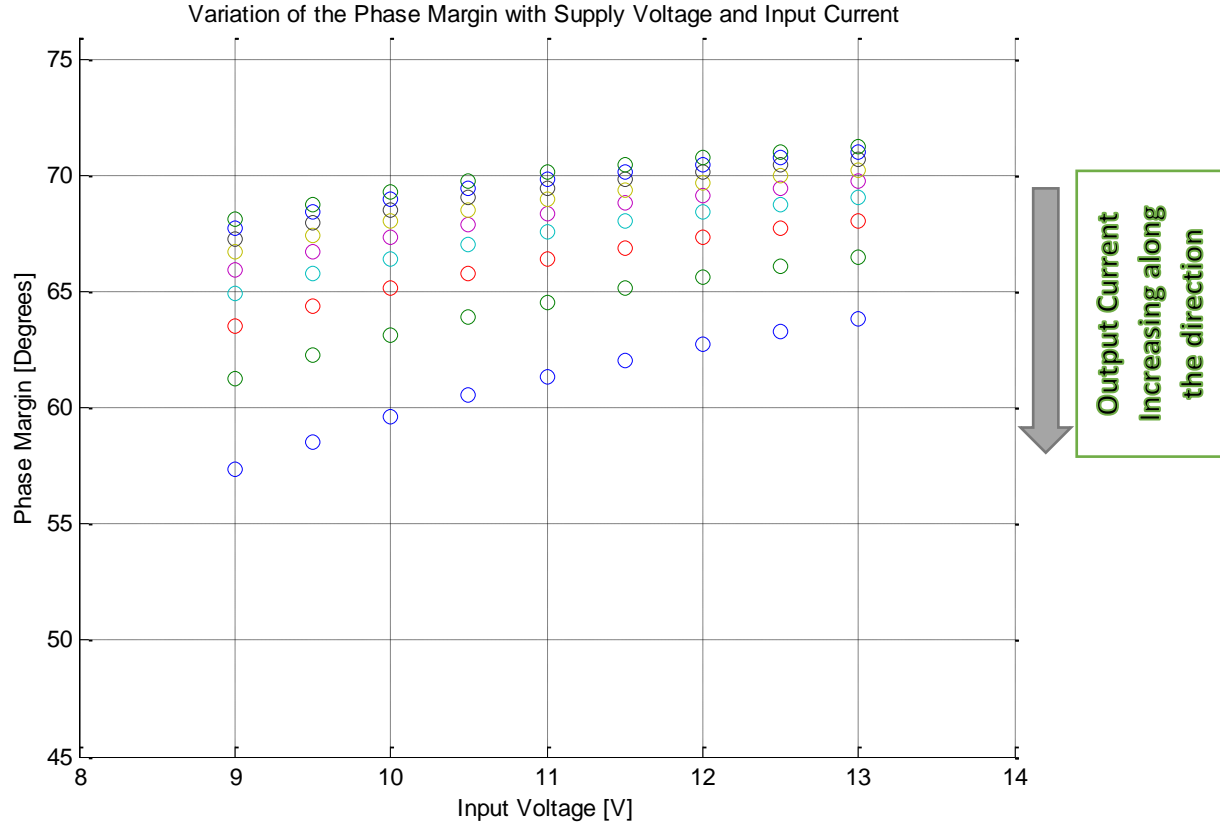


Figure 12: variation of the phase-margin with input voltage and load

Based on the above compensator, the full closed-loop system is tested in simulation. The system is tested with a load step response having the following characteristic:

 


Figure 13: load step for controller test

Here, t_{step} is a step time that is designed to be longer than the settling time, and t_{rep} is a given step repetition time ($t_{rep} = \frac{1}{50Hz} = 20ms$).

To achieve the above response the resistor varied from:

$$R_1 = \frac{V_o}{I_{out}} = \frac{32V}{0.5A} = 64\Omega$$

to:

$$R_2 = \frac{V_o}{I_{out}} = \frac{32V}{1A} = 32\Omega$$

and back.

Testing with such a step in simulation using the Simulink model given in Figure 11, one obtains the following result:

 


Figure 14: Load step response of the closed loop system

The voltage overshoot is up to 32.42V, and undershoot is down to 31.67V, for a steady-state voltage of 32V. This is within the range requirements (29.5V-34.6V), so this controller meets the specification.

Figure 15 shows experimental load step response of the controller from 160 Ω (0.2 A) to 80 Ω (0.4A) using the electronic load. The output voltage settles to the controlled value within 3ms. The sharp falling edge of the transient response of the above plot shows that the impact of the equivalent series resistance on the response of the controller is significant. Deviation of the voltage from the controlled value is limited to approximately 700mV.

 


Figure15: Experimental result for load step 160Ω to 180Ω .

Please note that unfortunately, we were unable to plot the controller response for the resistance step of 80Ω to 160Ω on the same plot as the above, since our gate driver for the load step is not functioning properly.

For a resistance step of 160Ω to 32Ω the result shown in Figure 16 was obtained. The result shows that there is a significant delay in the transient response of the controller. As it can be clearly seen from the figure there are spikes/noises. These can be potentially due to the Electromagnetic interference during probing (since the controller is clearly not responding to these changes although they are within the sensor bandwidth).

 


Figure 16: Experimental result for load step 60Ω to 32Ω

Remark and Conclusion

A reasonably fully operational converter with a digital controller was successfully designed. However, there were challenges in the process of designing both the hardware and software components. The list of issues raised during the project are given below:

- 1) *Ringings at the gate driver*: this was a main issue particularly at the beginning of the project, the high-side MOSFET was damaged once. Initially we had 5Ω gate resistors, but due to ringing issues these values had to be increased to a gate resistance of 10Ω for the low-side switch and 30Ω for the high-side switch (the inductance of the bootstrapping capacitor might have increased the ringing for the high-side MOSFET). We used sockets for the MOSFETs and the inductance of the sockets might have contributed to the increased ringing.
- 2) *Issue with gate driver*: in this project about 3 different gate driver were damaged. Two gate drivers were destroyed during closed loop testing of the final digital controller.
- 3) *Short circuits*: there were many incidents of shorting in the circuit due to soldering issues and also failure of the MOSFETs.
- 4) *Working with FPGA*: implementing the designed controller in FPGA was a big challenge, in particular operation with signed numbers in FPGA caused many problems and it required a long and time consuming debugging of the code.
- 5) *Soldering ADC and Buffer*: soldering these components required sharp soldering iron tip or hot air gun which were not easily accessible in the lab.

 


Figure 17: the designed boost converter

Reference

[1] Silicon Labs, "AN486: High-Side Bootstrap Design Using ISO Drivers in Power Delivery Systems".
Available at: <https://www.silabs.com/documents/public/application-notes/AN486.pdf>

Appendix A

Small signal modelling of the designed boost converter

For $0 < t < d(t)T_s$:

$$v_L(t) = v_g(t) - i_L(t)R_L - i_L(t)R_{ON}$$

$$i_c(t) = -\frac{v_o(t)}{R}$$

$$i_g(t) = i_L(t)$$

For $d(t)T_s < t < T_s$:

$$v_L(t) = v_g(t) - i_L(t)R_L - i_L(t)R_{ON} - v_o(t)$$

$$i_c(t) = i_L(t) - \frac{v_o(t)}{R}$$

$$i_g(t) = i_L(t)$$

The averaged model is:

$$\langle v_L(t) \rangle = d(t)(\langle v_g(t) \rangle - \langle i_L(t) \rangle R_L - \langle i_L(t) \rangle R_{ON}) + d'(t)(\langle v_g(t) \rangle - \langle i_L(t) \rangle R_L - \langle i_L(t) \rangle R_{ON} - \langle v_o(t) \rangle)$$

$$\langle i_c(t) \rangle = d(t)\left(-\langle \frac{v_o(t)}{R} \rangle\right) + d'(t)\left(\langle i_L(t) \rangle - \langle \frac{v_o(t)}{R} \rangle\right)$$

$$\langle i_g(t) \rangle = \langle i_L(t) \rangle$$

Perturbing and linearizing these equations:

$$L \frac{d(I_L + \hat{i}_L)}{dt} = (D + \hat{d})(V_g + \hat{v}_g - (I_L + \hat{i}_L)R_L - (I_L + \hat{i}_L)R_{ON}) + (D - \hat{d})(V_g + \hat{v}_g - (I_L + \hat{i}_L)R_L - (I_L + \hat{i}_L)R_{ON} - (V_o + \hat{v}_o))$$

$$C \frac{d(V_o + \hat{v}_o)}{dt} = (D + \hat{d})\left(-\frac{V_o + \hat{v}_o}{R}\right) + (D - \hat{d})\left((I_L + \hat{i}_L) - \frac{V_o + \hat{v}_o}{R}\right)$$

$$I_g + \hat{i}_g = I_L + \hat{i}_L$$


Removing the DC components and 2nd order terms, one obtains the AC small-signal dynamics:

$$L \frac{d\hat{i}_L}{dt} = \hat{v}_g + \hat{i}_L(R_L + R_{ON}) - D'\hat{v}_o + V_o\hat{d}$$

$$C \frac{\widehat{v_o}}{dt} = -\widehat{d}I_L + D'\widehat{i_L} - \frac{\widehat{v_o}}{R}$$

$$\widehat{i_g} = \widehat{i_L}$$

 Upon taking the Laplace transforms, the equivalent circuit models are:



Setting all other perturbation set to zero, and solving for $G_{vd}(s) = \frac{\widehat{v_o}}{\widehat{d}}$, the transfer function becomes:

$$G_{vd}(s) = \frac{\frac{1}{sC} || R \left(\frac{V_o}{D'} \right)}{\frac{1}{sC} || R + \frac{sL}{D'^2} + \frac{R + R_{on}}{D'^2}} - I_L \left(\frac{sL}{D'^2} + \frac{R + R_{on}}{D'^2} \right) || \frac{1}{sC} || R$$

The control to output transfer function of the system including the equivalent series resistance of the output capacitor is given below.

$$G_{vd} = \frac{\left(\frac{1}{sC} + R_{ESR} \right) || R \left(\frac{V_o}{D'} \right)}{\left(\frac{1}{sC} + R_{ESR} \right) || R + \frac{sL}{D'^2} + \frac{R + R_{on}}{D'^2}} - I_L \left(\frac{sL}{D'^2} + \frac{R + R_{on}}{D'^2} \right) || \left(\frac{1}{sC} + R_{ESR} \right) || R$$

Appendix B: input Voltage Sensing

Similar to the output voltage, the input voltage sensor also has the same configuration with the low pass filter. The DC gain is:

$$K_{sense} = \frac{R_9}{R_9 + R_{10}}$$

With the input voltage being at most 14V, this voltage must be stepped down to the level of the ADC. Because a signed value is not needed for the input voltage to indicate deviation away from a mid-

range value (i.e. it is not used in the linear control loop as an error), it suffices to just step down the maximum voltage to 5V. Hence, the DC gain is:

$$K_{sense} = \frac{R_9}{R_9 + R_{10}} = \frac{5V}{14V}$$

To design this, the resistors chosen are then $R_9 = 50k\Omega$ and $R_{10} = 100k\Omega$, approximately achieving this ratio.

The pole for the filter is still the same form:

$$\omega_{sense} = \frac{1}{C_1(R_9 || R_{10})}$$

This time, however, the pole must only be placed so that the signal being sampled by the ADC is not aliased as a result of the sampling. Based on a sampling rate of $f_{samp} = 250kHz$, the Nyquist frequency is $f_{Ny} = 125kHz$. The signal must be significantly attenuated at this frequency to avoid aliasing and remove high frequency, so the pole is placed at a significantly lower. Choosing a low pole frequency of $f_{sense} = 5kHz$ based on the components available, a suitable capacitance of:

$$\begin{aligned} C_1 &= \frac{1}{2\pi(R_9 || R_{10})} \\ &= 1nF \end{aligned}$$

can be used.

Appendix C:

Code used for testing the converter.

```

1  //MAIN
2
3  module DPWM (
4      input [17:0] SW          // Selection Bits
5      //, input [RESOLUTION-1:0] SW // Value Bits
6      , input [3:0] KEY
7      , input CLOCK_50
8
9      , inout [35:0] GPIO_0
10     , output [35:0] GPIO_1
11     , output [3:0] LEDG
12     , output [17:0] LEDR
13 );
14
15 wire adc_CLK;
16
17 pll DPWM_PLL (
18     .inclk0(CLOCK_50),
19     .cl(adc_CLK),
20 );
21
22
23 wire [15:0] adc_output;
24 spi ad7324(
25     .DOUT(GPIO_0[1]),
26     .CLK_IN(adc_CLK),
27     .R(KEY[3]),
28     .HOLD(CLK1MHz),
29     .READ_ALL(1'b0),
30
31     .DIN(GPIO_0[7]),
32     .CS(GPIO_0[5]),
33     .CLK_OUT(GPIO_0[3]),
34     .DATA_READ(adc_output)
35 );
36 //assign LEDR[15:0] = adc_output;
37
38 reg [9:0] maxcount;
39 always@ (*)
40     case (SW[3:0])
41
42         4'b0000: maxcount=10'b1111101000;//1000 and freq = 50khz
43         4'b0001: maxcount=10'b1100000001;//769 and freq = 65khz
44         4'b0010: maxcount=10'b1001110001;//625 and freq = 80khz
45         4'b0011: maxcount=10'b1000001110;//526 and freq = 95khz
46         4'b0101: maxcount=10'b0110010000;//400 and freq = 125khz
47         4'b0110: maxcount=10'b0101100101;//357 and freq = 140khz
48         4'b1011: maxcount=10'b0101001110;//334 and freq =
150khz
49         4'b0111: maxcount=10'b0101000010;//322 and freq = 155khz
50         4'b1000: maxcount=10'b0100100110;//294 and freq = 170khz
51         4'b1001: maxcount=10'b0100001110;//270 and freq = 185khz
52         4'b1010: maxcount=10'b0011111010;//250 and freq = 200khz
53         default: maxcount=10'b1111101000;
54     endcase
55
56
57 wire S1, S2;
58
59
60 assign GPIO_0[32] = S1;
61 assign GPIO_0[34] = S2;
62
63
64 wire CLK1MHz;
65 //clock divider for the ADC input

```

```

66 clk_divider GET_1MHz(
67   .clk(adc_CLK),
68   .reset(0),
69   .clk_out(CLK1MHz)
70 );
71
72 wire CLK10kHz;
73 //clock divider for the ADC input
74 clk_divider_10kHz GET_10kHz(
75   .clk(CLK1MHz),
76   .reset(0),
77   .clk_out(CLK10kHz)
78 );
79
80
81 assign GPIO_1[32] = CLK10kHz;
82
83
84
85 //Soft start
86 reg [7:0]Duty_Cycle;
87 //The following code pertains to the Controller
88 reg [1:0]identifier;
89 reg [11:0]Temp, Vin, Iin;
90 reg signed [59:0]Vout;
91 reg [59:0]controller_DC;
92 reg signed[59:0]V_ref;
93 reg signed [59:0]V_error, V_error1, V_error2;
94
95 reg signed [59:0]out_DC, DC1k;
96
97
98 always@ (posedge CLK10kHz)
99 begin
100   identifier <= adc_output[14:13];
101   V_ref <= $signed(60'b0011111100); // dropped the last 4 bits from 60'b00101101001101
102   Vout <= $signed(adc_output[12:4]);
103
104   if(identifier==2'b00)
105
106
107   //2 controllers were developed, as shown below. Only Type 2 was ultimately selected
108   //Using TYPE 2 CONTROLLER (PI)
109   begin
110
111     V_error = (V_ref - Vout); //255 ADC gain
112
113     if (SW[17]==1) begin
114       out_DC =60'b0011111100*255;
115     end
116     else begin
117       out_DC = (DC1k*524288 + 16811*V_error);
118       out_DC = out_DC>>>19; //dividing by 524288
119       if(out_DC > 60'b01011010001011011) begin
120         out_DC =60'b0011111100*255; //since it will end up beign devided
121       end
122       DC1k = out_DC;
123
124     end
125   end
126
127   //TYPE 1 CONTROLLER (PID)
128   /* begin
129
130     Vout <= 0; //Vout <= adc_output[11:3];
131     V_error = (V_ref - Vout); //255 ADC gain

```

```

132     controller_DC = 334*((11181*DC1k) - (1181*DC2k) +
133       ((100000*V_error)-(199500*V_error1)+(99510*V_error2))); //334 DPWM gain
134
135     //Setting History terms
136     if (controller_DC > 60'b1111100000000110011111010000) begin //the value of
137       controller_DC should not exceed (130050000) or 1111100000000110011111010000
138
139       controller_DC = 60'b1; //60'b1111100000000110011111010000
140       DC2k <=DC1k;
141       DC1k <=controller_DC;
142       V_error2 <=V_error1;
143       V_error1 <=V_error;
144
145     end
146     else begin
147       DC2k <=DC1k;
148       DC1k <=controller_DC;
149       V_error2 <=V_error1;
150       V_error1 <=V_error;
151
152     end */
153
154
155
156
157     end // identifier for cases 2'b01, 2'b10 and 2'b11
158
159
160     wire [59:0] quotient; //Value of quotient should not exceed 255
161
162     division (out_DC, 60'b011111111, quotient); //dividing by 255
163
164
165     //here assign quotient[9:0] to duty Cycle
166     gating (.CLK_50(CLOCK_50), .DutyCycle(quotient[7:0]), .maxcount(10'b0101001110), .reset
167       (KEY[0]), .SET(KEY[1]), .S1(S1), .S2(S2));
168
169 endmodule
170
171
172
173 module gating(CLK_50, DutyCycle, maxcount, reset, SET, S1, S2);
174
175     input [9:0]DutyCycle, maxcount;
176     input reset, SET, CLK_50;
177     output S1, S2;
178     reg [9:0] counter; //is this initialized to zero by default???
179     reg C_1, C_2; //temporary variables
180     always @(posedge CLK_50, negedge reset)
181     begin
182         if (!reset)
183         begin
184             C_1<=0;
185             C_2<=0;
186             counter = 10'b0;
187         end
188         else if(!SET)
189         begin
190             C_1<=0;
191             C_2<=0;
192         end
193         else
194         begin

```

```

195         if (counter < maxcount) // at every 0.5 seconds, activate
196             counter = counter + 1;
197         else
198             counter = 0;
199         //the duty cycle adjusted based on the switch input
200         if (counter > DutyCycle)
201             begin
202                 C_2<=1'b0;
203                 C_1 <= 1'b1;
204             end
205         else
206             begin
207                 C_1<=1'b0;
208                 C_2 <= 1'b1;
209             end
210         end
211     end
212 end
213
214 wire bit_value1, bit_value2;
215
216
217
218 shiftm forDT1(3'b110, C_1, CLK_50, bit_value1);
219 shiftm forDT2(3'b110, C_2, CLK_50, bit_value2);
220
221 assign S2 = bit_value1 && C_1;
222 assign S1 = bit_value2 && C_2;
223
224 endmodule
225
226
227
228 module shiftm (binary, w, Clock, bit_value);
229 input [2:0]binary;
230 integer n;
231 always@ (binary)
232     case (binary)
233
234         3'b001: n=0;
235         3'b010: n=1;
236         3'b011: n=2;
237         3'b100: n=3;
238         3'b101: n=4;
239         3'b110: n=5;
240         default: n=0;
241     endcase
242
243
244 input w, Clock;
245
246 reg [5:0]Q;
247 integer k;
248 output reg bit_value;
249 always @(posedge Clock)
250     begin
251         for (k = 0; k < 5; k = k+1)
252             Q[k] <= Q[k+1];
253
254         Q[n] <= w;
255         bit_value <= Q[0];
256     end
257 endmodule
258
259
260 module DutyCycleConverter (SW_value, clk2, frequency, duty);

```



```

261 input clk2;
262 input [3:0] frequency;
263 input [7:0] SW_value;
264 output reg [9:0] duty;
265
266 always@ (*)
267     case (frequency)
268
269         4'b0000: duty = SW_value*8'b0000_0100;//1000 and freq = 50khz
270         4'b0001: duty = SW_value*8'b0000_0100;//769 and freq = 65khz
271         4'b0010: duty = SW_value*8'b0000_0100;//625 and freq = 80khz
272         4'b0011: duty = SW_value*8'b0000_0100;//526 and freq = 95khz
273         4'b0100: duty = SW_value*8'b0000_0010;//455 and freq = 110khz
274         4'b0101: duty = SW_value*8'b0000_0010;//400 and freq = 125khz
275         4'b0110: duty = SW_value*8'b0000_0010;//357 and freq = 140khz
276         4'b0111: duty = SW_value*8'b0000_0010;//322 and freq = 155khz
277         4'b1000: duty = SW_value*8'b0000_0010;//294 and freq = 170khz
278         4'b1001: duty = SW_value*8'b0000_0010; //270 and freq = 185khz
279         4'b1010: duty = SW_value*8'b0000_0001; //250 and freq = 200khz, whe should not
                go beyond 250!!!!!!!
280
281         default: duty = SW_value*8'b0000_0100;
282     endcase
283 endmodule
284
285
286 module deadtime_generator #(parameter RESOLUTION = 12)
287 (
288     input wire hf_clock
289     , input wire [RESOLUTION-1:0] hs_deadtime
290     , input wire [RESOLUTION-1:0] ls_deadtime
291     , input wire HPWM
292     , input wire LPWM
293     , input wire reset
294
295     , output wire pwm
296     , output wire cpwm
297 );
298
299 //WIRES
300 wire [RESOLUTION-1:0] hs_dt_counter;
301 wire [RESOLUTION-1:0] ls_dt_counter;
302 wire deadtime_hs_mask = hs_dt_counter >= hs_deadtime;
303 wire deadtime_ls_mask = ls_dt_counter >= ls_deadtime;
304
305 positive_counter #( .WIDTH(RESOLUTION) ) HS_DT_CTR (
306     .clk(hf_clock),
307     .reset(~HPWM | reset),
308     .enable(1'b1),
309     .count(hs_dt_counter)
310 );
311
312 positive_counter #( .WIDTH(RESOLUTION) ) LS_DT_CTR (
313     .clk(hf_clock),
314     .reset(~LPWM | reset),
315     .enable(1'b1),
316     .count(ls_dt_counter)
317 );
318
319 assign pwm = (HPWM & deadtime_hs_mask) & (~reset);
320 assign cpwm = (LPWM & deadtime_ls_mask) & (~reset);
321
322 endmodule
323
324 //

```

[Reference://http://verilogcodes.blogspot.ca/2015/11/synthesizable-verilog-code-for-divisi](http://verilogcodes.blogspot.ca/2015/11/synthesizable-verilog-code-for-divisi)

```

325 on_html
326 module division(A, B, Res);
327 //the size of input and output ports of the division module is generic.
328 parameter WIDTH = 40;
329 //input and output ports.
330 input [WIDTH-1:0] A;
331 input [WIDTH-1:0] B;
332 output [WIDTH-1:0] Res;
333 //internal variables
334 reg signed [WIDTH-1:0] Res = 0;
335 reg signed [WIDTH-1:0] al,bl;
336 reg signed [WIDTH:0] pl;
337 integer i;
338
339 always@ (A or B)
340 begin
341 //initialize the variables.
342 al = A;
343 bl = B;
344 pl = 0;
345 for(i=0;i < WIDTH;i=i+1) begin //start the for loop
346 pl = {pl[WIDTH-2:0],al[WIDTH-1]};
347 al[WIDTH-1:1] = al[WIDTH-2:0];
348 pl = pl-bl;
349 if(pl[WIDTH-1] == 1) begin
350 al[0] = 0;
351 pl = pl + bl; end
352 else
353 al[0] = 1;
354 end
355 Res = al;
356 end
357
358 endmodule
359
360 module input_sanitizer #( parameter RESOLUTION = 12 ) (
361 input wire [RESOLUTION-1:0] dc
362 , input wire [RESOLUTION-1:0] fs
363 , input wire [RESOLUTION-1:0] dt1
364 , input wire [RESOLUTION-1:0] dt2
365
366 , output wire [RESOLUTION-1:0] san_dc
367 , output wire [RESOLUTION-1:0] san_fs
368 , output wire [RESOLUTION-1:0] san_dt1
369 , output wire [RESOLUTION-1:0] san_dt2
370 );
371
372 // WIRES
373 wire [RESOLUTION-1:0] fs_inv;
374
375 // MAIN CODE
376
377 // Frequency Select Sanitization
378 assign fs_inv = {RESOLUTION{1'b1}} - fs;
379 assign san_fs = (fs_inv < 2) ? 2 : fs_inv;
380
381 // Duty Cycle Sanitization
382 assign san_dc = (dc > san_fs) ? san_fs : dc;
383
384 // Deadtime1 Sanitization
385 assign san_dt1 = (dt1 > san_dc) ? san_dc : dt1;
386
387 // Deadtime2 Sanitization
388 assign san_dt2 = (dt2 > (san_fs - san_dc)) ? (san_fs - san_dc) : dt2;

```

```

390
391     endmodule
392
393
394     module clk_divider #(parameter WIDTH = 5, parameter N = 20) (
395     input clk,
396     input reset,
397     output clk_out);
398
399
400     //input clk;
401     //input reset;
402     //output clk_out;
403
404     reg [WIDTH-1:0] pos_count, neg_count;
405     wire [WIDTH-1:0] r_nxt;
406
407     always @(posedge clk)
408     if (reset)
409     pos_count <=0;
410     else if (pos_count ==N-1) pos_count <= 0;
411     else pos_count<= pos_count +1;
412
413     always @(negedge clk)
414     if (reset)
415
416     neg_count <=0;
417
418     else if (neg_count ==N-1) neg_count <= 0;
419
420     else neg_count<= neg_count +1;
421
422     assign clk_out = ((pos_count > (N>>1)) | (neg_count > (N>>1)));
423
424     endmodule
425
426     module clk_divider_10kHz #(parameter WIDTH = 7, parameter N = 100) (
427     input clk,
428     input reset,
429     output clk_out);
430
431
432     //input clk;
433     //input reset;
434     //output clk_out;
435
436     reg [WIDTH-1:0] pos_count, neg_count;
437     wire [WIDTH-1:0] r_nxt;
438
439     always @(posedge clk)
440     if (reset)
441     pos_count <=0;
442     else if (pos_count ==N-1) pos_count <= 0;
443     else pos_count<= pos_count +1;
444
445     always @(negedge clk)
446     if (reset)
447
448     neg_count <=0;
449
450     else if (neg_count ==N-1) neg_count <= 0;
451
452     else neg_count<= neg_count +1;
453
454     assign clk_out = ((pos_count > (N>>1)) | (neg_count > (N>>1)));
455

```

```

456 endmodule
457
458 module clk_divider_100Hz #(parameter WIDTH = 19, parameter N = 500000) (
459 input clk,
460 input reset,
461 output clk_out);
462
463
464 //input clk;
465 //input reset;
466 //output clk_out;
467
468 reg [WIDTH-1:0] pos_count, neg_count;
469 wire [WIDTH-1:0] r_nxt;
470
471 always @(posedge clk)
472 if (reset)
473 pos_count <= 0;
474 else if (pos_count == N-1) pos_count <= 0;
475 else pos_count <= pos_count + 1;
476
477 always @(negedge clk)
478 if (reset)
479
480 neg_count <= 0;
481
482 else if (neg_count == N-1) neg_count <= 0;
483
484 else neg_count <= neg_count + 1;
485
486 assign clk_out = ((pos_count > (N>>1)) | (neg_count > (N>>1)));
487
488 endmodule
489
490
491
492
493
494
495
496
497 module LCD_display(
498 input CLOCK_50, // 50 MHz clock
499 input [1:0] KEY, // Pushbutton[0]
500 input [1:0] SW, //Using 2 switches
501 output [6:0] HEX0,HEX1,HEX2,HEX3,HEX4,HEX5,HEX6,HEX7, // Seven Segment Digits
502 input [3:0] VinH,VinL,VoutH,VoutL,IoutH,IoutL,TempH,TempL,
503 //output [1:0] LEDR, // LED Red
504 // LCD Module 16X2
505 output LCD_ON, // LCD Power ON/OFF
506 output LCD_BLON, // LCD Back Light ON/OFF
507 output LCD_RW, // LCD Read/Write Select, 0 = Write, 1 = Read
508 output LCD_EN, // LCD Enable
509 output LCD_RS, // LCD Command/Data Select, 0 = Command, 1 = Data
510 inout [7:0] LCD_DATA // LCD Data bus 8 bits
511 );
512 //Add reset button
513 wire RST;
514 assign RST = ~KEY[0]; //KEY 0 for reset (key is normally high)
515
516 // reset delay gives some time for peripherals to initialize
517 wire DLY_RST;
518 Reset_Delay r0( .iCLK(CLOCK_50),.oRESET(DLY_RST) );
519
520 // Send switches to red leds
521 //assign LEDR = SW[1:0];

```

```

522
523 // turn LCD ON
524 assign LCD_ON = 1'b1;
525 assign LCD_BLON = 1'b1;
526
527 //Take ADC input
528 //OPTION1: 8 bits x 4 measurements
529 //Will write to each output unit as hex character, not bit, so padded with 3 zeros at
start
530 /* reg [3:0] hex[31:0]; //32 output units, each a hex character
531 wire [3:0] output[31:0];
532 integer i, j;
533 always@(*) begin
534     for (i = 0; i < 3; i = i + 1) begin
535         hex[i][0]=VinL[i];
536         for (j = 1; j < 3; j = j + 1) begin
537             hex[i][j]=1'b0;
538         end
539     end
540 end
541 assign output=hex; */
542
543 wire [3:0] hex0, hex1, hex2, hex3, hex4, hex5, hex6, hex7;
544 //OPTION2: 2 hex x 4 measurement (+names)
545 assign hex0 = VinL; assign hex1 = VinH; assign hex2 = VoutL; assign hex3 = VoutH; assign
hex4 = IoutL;
546 assign hex5 = IoutH; assign hex6 = TempL; assign hex7 = TempH;
547
548 LCD_Display ul(
549 // Host Side
550 .iCLK 50MHZ(CLOCK 50),
551 .iRST_N(DLY_RST),
552 .hex0(hex0), .hex1(hex1), .hex2(hex2), .hex3(hex3),
553 .hex4(hex4), .hex5(hex5), .hex6(hex6), .hex7(hex7),
554 // LCD Side
555 .DATA_BUS(LCD_DATA),
556 .LCD_RW(LCD_RW),
557 .LCD_E(LCD_EN),
558 .LCD_RS(LCD_RS)
559 );
560
561
562 // blank unused 7-segment digits
563 assign HEX0 = 7'b111_1111; assign HEX1 = 7'b111_1111; assign HEX2 = 7'b111_1111;
564 assign HEX3 = 7'b111_1111; assign HEX4 = 7'b111_1111; assign HEX5 = 7'b111_1111;
565 assign HEX6 = 7'b111_1111; assign HEX7 = 7'b111_1111;
566
567 endmodule
568
569 `ifndef CUSTOM_LCD_DISPLAY_STRING
570 module LCD_display_string(index,out,hex0,hex1,hex2, hex3, hex4, hex5, hex6, hex7);
571 input [4:0] index;
572 input [3:0] hex0, hex1, hex2, hex3, hex4, hex5, hex6, hex7;
573 output [7:0] out;
574 reg [7:0] out;
575 // ASCII hex values for LCD Display
576 // Enter Live Hex Data Values from hardware here
577 // LCD DISPLAYS THE FOLLOWING:
578 //-----
579 //| Vin=hh Vout=hh |
580 //| Iout=hh Temp=hh |
581 //-----
582
583 /*--
584 -- Hex ASCII HEX TABLE
585 -- Value 0 1 2 3 4 5 6 7 8 9 A B C D E F

```

```

586  -----\
587  --H 2 | SP ! " # $ % & ' ( ) * + , - . /
588  --i 3 | 0 1 2 3 4 5 6 7 8 9 : ; < = > ?
589  --g 4 | @ A B C D E F G H I J K L M N O
590  --h 5 | P Q R S T U V W X Y Z [ \ ] ^ _
591  -- 6 | ` a b c d e f g h i j k l m n o
592  -- 7 | p q r s t u v w x y z { | } ~ DEL
593  -----
594  -- Example "A" is row 4 column 1, so hex value is 8'h41"
595  -- *see LCD Controller's Datasheet for other graphics characters available
596  */
597
598  // Line 1
599  always
600      case (index)
601          5'h00: out <= 8'h56;
602          5'h01: out <= 8'h69;
603          5'h02: out <= 8'h6E;
604          5'h03: out <= 8'h3D;
605          5'h04: out <= {4'h0,hex1};
606          5'h05: out <= {4'h0,hex0};
607          5'h06: out <= 8'h56;
608          5'h07: out <= 8'h6F;
609          5'h08: out <= 8'h75;
610          5'h09: out <= 8'h74;
611          5'h0A: out <= 8'h3D;
612          5'h0B: out <= {4'h0,hex3};
613          5'h0C: out <= {4'h0,hex2};
614  // Line 2
615          5'h10: out <= 8'h49;
616          5'h11: out <= 8'h6F;
617          5'h12: out <= 8'h75;
618          5'h13: out <= 8'h74;
619          5'h14: out <= 8'h3D;
620          5'h15: out <= {4'h0,hex5};
621          5'h16: out <= {4'h0,hex4};
622          5'h17: out <= 8'h54;
623          5'h18: out <= 8'h65;
624          5'h19: out <= 8'h6D;
625          5'h1A: out <= 8'h70;
626          5'h1B: out <= 8'h3D;
627          5'h1C: out <= {4'h0,hex7};
628          5'h1D: out <= {4'h0,hex6};
629          default: out <= 8'h20;
630      endcase
631  endmodule
632
633  `endif
634
635
636
637
638  module Reset_Delay(iCLK,oRESET);
639  input iCLK;
640  output reg oRESET;
641  reg [19:0] Cont;
642
643  always@(posedge iCLK)
644  begin
645      if(Cont!=20'hFFFFFF)
646      begin
647          Cont <= Cont+1'b1;
648          oRESET <= 1'b0;
649      end
650      else
651          oRESET <= 1'b1;

```

```
652     end
653
654     endmodule
655
```